

## **EECS 119**

### **Project #1**

#### **Inverter and Oscillator**

1. Design an inverter to get  $N_{MH}=N_{ML}$  and  $T_{PLH}=T_{PHL}$ . Draw the **layout** of the designed inverter.
2. Obtain the noise margins and the propagation delay time by simulating the **layout** and plotting dynamic and static characteristics.
3. Design an oscillator by placing 5 inverters designed above in a closed loop.
4. Run a simulation and plot the waveform at the output of each node. Compare the frequency of the generated signal with the expected frequency based upon the obtained  $t_p$  of the inverter.

Report: Submit the layout, results of the simulation, design calculations, etc. in the form of a report.

Deadline: Two Weeks