

EECS 119: Design Project 3

Design of a Four Bit Adder/Subtractor

1. Given two 4-bit positive binary numbers A and B, you are to design an adder/subtractor circuit to compute $(A+B)$ or $(A-B)$, depending upon a mode input which controls the operation. You may use one's or two's complement of B to perform subtraction. The result with the proper sign is to be displayed in un-complemented binary form.
2. Obtain complete **layout** of the designed circuit.
3. Simulate the **layout** and demonstrate that the layout works and generates the correct output.
4. You may work in groups with each group containing at most two students.
5. Submit a report containing:
 - a. Cover sheet.
 - b. Designed circuit.
 - c. Complete layout.
 - d. Sample results of the simulation.
6. Demonstrate the project to teaching assistant.

Teaching assistants will inform you of details about project submission and demonstration.